

TED (15) - 3044

(REVISION --- 2015)

https://mail.gptcthirurangadi.in

Reg. No	
Signature	

DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/ MANAGEMENT/COMMERCIAL PRACTICE — APRIL, 2019

ELECTRONIC DEVICES AND CIRCUITS

[*Time* : 3 hours

(Maximum marks : 100)

PART — A

(Maximum marks : 10)

Marks

 $(5 \times 2 = 10)$

I Answer all questions in one or two sentences. Each question carries 2 marks.

- 1. List different methods of inter stage coupling in amplifiers.
- 2. Write an expression for resonant frequency of resonant circuits.
- 3. Define piezo electric effect.
 - 4. State Barkhausen criterion for oscillation.
 - 5. List types of negative feedback in amplifiers.

PART — B

(Maximum marks : 30)

II Answer any *five* of the following questions. Each question carries 6 marks.

- 1. Explain emitter follower with the help of diagram.
- 2. Explain the effects of negative feedback in amplifiers.
- 3. Compare BJT and FET.
- 4. Explain importance of impedance matching in power amplifier.
- 5. Draw the circuit diagram of direct coupled amplifier and explain.
- 6. Explain importance of heat sink in power amplifier.
- 7. Draw and explain RC differentiating circuit with waveforms.



2

PART — C

(Maximum marks : 60)

(Answer one full question from each unit. Each full question carries 15 marks.)

Unit — I

III	(a)	Explain the principle of operation of transistor amplifier in Common emitter configuration.	8
	(b)	Explain frequency response of RC coupled amplifier.	7
		Or	
IV	(a)	Write expression for voltage gain, current gain, power gain, input and output impedances of common emitter amplifier.	8
	(b)	Draw and explain transformer coupled amplifier.	7
		Unit — II	
V	(a)	Draw and explain the circuit of complimentary push pull amplifier.	8
	(b)	Explain frequency response of single tuned amplifier and write Relation between resonant frequency, bandwidth and Q factor.	7
		Or	
VI	(a)	Classify power amplifiers with the help of proper diagrams.	8
	(b)	Draw and explain single tuned amplifier circuit.	7
		Unit — III	
VII	(a)	Derive an expression for feedback in amplifiers.	8
	(b)	Explain the working principle of JFET.	7
		Or	
VIII	(a)	Explain the types of negative feedback in amplifiers with the help of diagrams.	8
	(b)	Draw and explain UJT relaxation oscillator.	7
		Unit — IV	
IX	(a)	Explain the working of RC phase shift oscillator with the help of diagram.	7
•	(b)	Explain the working of Schmitt trigger with the help of Circuit diagram and waveforms.	8
		Ûr	
Х	(a)	Draw and explain Hartley oscillator.	7
	(b)	Explain the operation of transistor astable multivibrator with the help of circuit	
		magram and wavelonns.	8

Marks