



N19-02201

TED (15) -3133

Reg. No. ....

(REVISION — 2015)

Signature .....

DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/  
MANAGEMENT/COMMERCIAL PRACTICE — OCTOBER, 2019

DIGITAL COMPUTER PRINCIPLES

[Time : 3 hours]

(Maximum marks : 100)

PART — A

(Maximum marks : 10)

Marks

I Answer *all* questions in one or two sentences. Each question carries 2 marks.

1. Define 2's complement of a number with example.
2. What is weighted binary code ? Give an example.
3. Define combinational logic.
4. List the asynchronous inputs of a flipflop.
5. Name any one error detection and correction code.

(5×2 = 10)

PART — B

(Maximum marks : 30)

II Answer any *five* of the following questions. Each question carries 6 marks.

1. Design two input AND and two input OR Operations using NAND gate.
2. State and prove Demorgan's laws.
3. Reduce the expression  $F = A + AB + ABC + ABCD$
4. Design and explain the circuit of a Half adder.
5. Draw and explain the circuit of a Clocked D Flip-flop
6. Draw the circuit of a 3 bit binary Up counter using JK Flip-Flop.
7. Define the terms Resolution and Accuracy of a DAC

(5×6 = 30)



PART — C

(Maximum marks : 60)

(Answer *one* full question from each unit. Each full question carries 15 marks.)

UNIT — I

III (a) Convert the following

(i)  $ABCD_{16}$  to OCTAL (ii)  $1000_{10}$  to Binary

(iii)  $476_8$  to Decimal

9

(b) Draw the logic diagram and truth table of two input NOR gate and EXOR gate.

6

OR

IV (a) Explain different Boolean laws and theorems.

9

(b) Draw the logic diagrams and truth tables of basic gates.

6

UNIT — II

V (a) Simplify using Kmap and draw the logic circuit for  
 $F_{(ABCD)} = \sum (0,1,2,3,6,7,8,9)$

9

(b) Define Minterms and Maxterms.

6

OR

VI (a) Draw and explain the circuit of a 4 bit binary adder.

9

(b) Draw the circuit and truth table of 4 to 1 Multiplexer.

6

UNIT — III

VII (a) Explain the basic operations of different shift registers with neat sketch.

9

(b) Draw the circuit of a 4 bit ring counter.

6

OR

VIII (a) Draw and explain the operations of Master Slave JK with truth table.

9

(b) Compare synchronous and asynchronous counter.

6

UNIT — IV

IX (a) Explain the working of a R-2R ladder type ADC with neat sketch.

9

(b) Define monotonicity and offset voltage.

6

OR

X (a) Explain the working of Counter type ADC with neat sketch.

9

(b) Explain the operation of reading and writing a memory cell.

6