



ED (21) 4043
(Revision – 2021)

A23-2103230123A

<https://mail.gptcthirurangadi.in>

Reg. No.....

Signature

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/
MANAGEMENT/COMMERCIAL PRACTICE, APRIL – 2023**

LINEAR INTEGRATED CIRCUITS

[Maximum Marks: 75]

[Time: 3 Hours]

PART-A

I. Answer *all* the following questions in one word or one sentence. Each question carries 'one' mark.

(9 x 1 = 9 Marks)

		Module Outcome	Cognitive level
1.	Draw equivalent circuit of op-amp.	M1.02	U
2.	Define CMRR.	M1.03	R
3.	List the op-amp package.	M1.02	R
4.	What is log amplifier?	M2.01	R
5.	List any two applications of comparator.	M2.04	R
6.	Define lock-in range.	M3.04	R
7.	Draw pin diagram of timer IC555.	M3.01	R
8.	Classify the IC voltage regulators.	M4.01	U
9.	Define resolution of ADC.	M4.02	R

PART-B

II. Answer any *eight* questions from the following. Each question carries 'three' marks.

(8 x 3 = 24 Marks)

		Module Outcome	Cognitive level
1.	Show op amp voltage follower as unity gain amplifier.	M1.04	U
2.	Explain Inverting Amplifier using op-amp.	M1.04	U
3.	Determine frequency of wien bridge oscillator for $C=0.05\mu F$ and $R=1.59K\Omega$.	M2.03	A
4.	Explain Half wave precision rectifier.	M2.02	U
5.	Explain Voltage to current converter.	M2.01	U
6.	Draw circuit diagram of monostable multivibrator using op amp.	M2.03	U
7.	Draw the circuit diagram of 555 timer is configured in monostable mode.	M3.02	U
8.	Draw functional block diagram of NE565 PLL IC.	M3.03	U
9.	List the features of voltage regulator IC 723.	M4.01	U
10.	Define Monotonicity, Settling time, Linearity.	M4.03	U



PART-C

Answer all questions. Each question carries 'seven' marks

(6 x 7 = 42 Marks)

		Module Outcome	Cognitive level
III.	List the op amp parameters and explain any five. OR	M1.03	U
IV.	Explain the working of BJT differential amplifier.	M1.01	U
V.	Explain the working Schmitt trigger using op amp. OR	M2.04	U
VI.	Construct a first order high-pass filter at a cut-off frequency of 2 kHz with a pass band gain of 2.	M2.05	A
VII.	Explain the working of triangular wave generator. OR	M2.03	U
VIII.	Explain working of clipper and clamper using op amp.	M2.02	U
IX.	Explain working of astable multivibrator using IC 555. OR	M3.02	U
X.	Explain the working of PLL as AM and FM detection.	M3.04	U
XI.	Explain the working principle of opto coupler. OR	M4.01	U
XII.	With the help of circuit diagram explain High Voltage Regulator using IC723.	M4.01	U
XIII.	Explain the working of weighted resistor type DAC. OR	M4.02	U
XIV.	Explain the working of dual slope ADC.	M4.03	U
